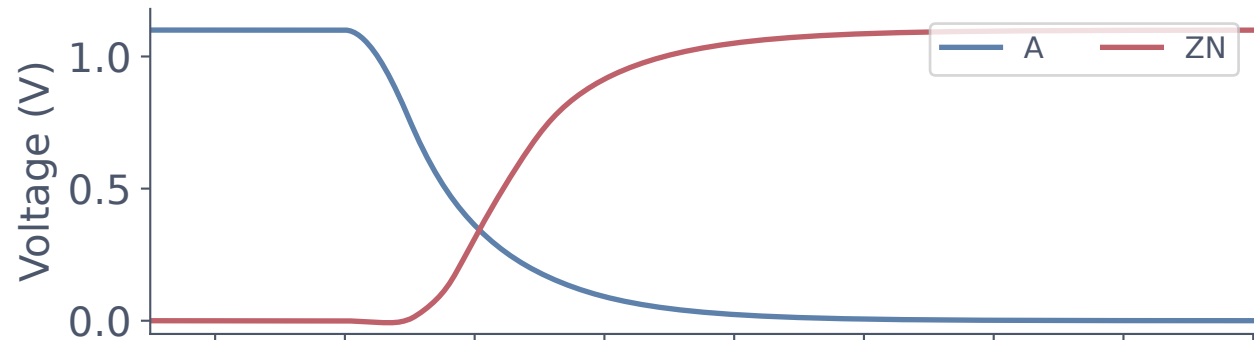


Output rises: VDD charges load



Output falls: load discharges

